


VLSI design Lab

Manish Ranjan


24M1176

A. Dadda Multiplier


1. Post Implementation Timing Simulation

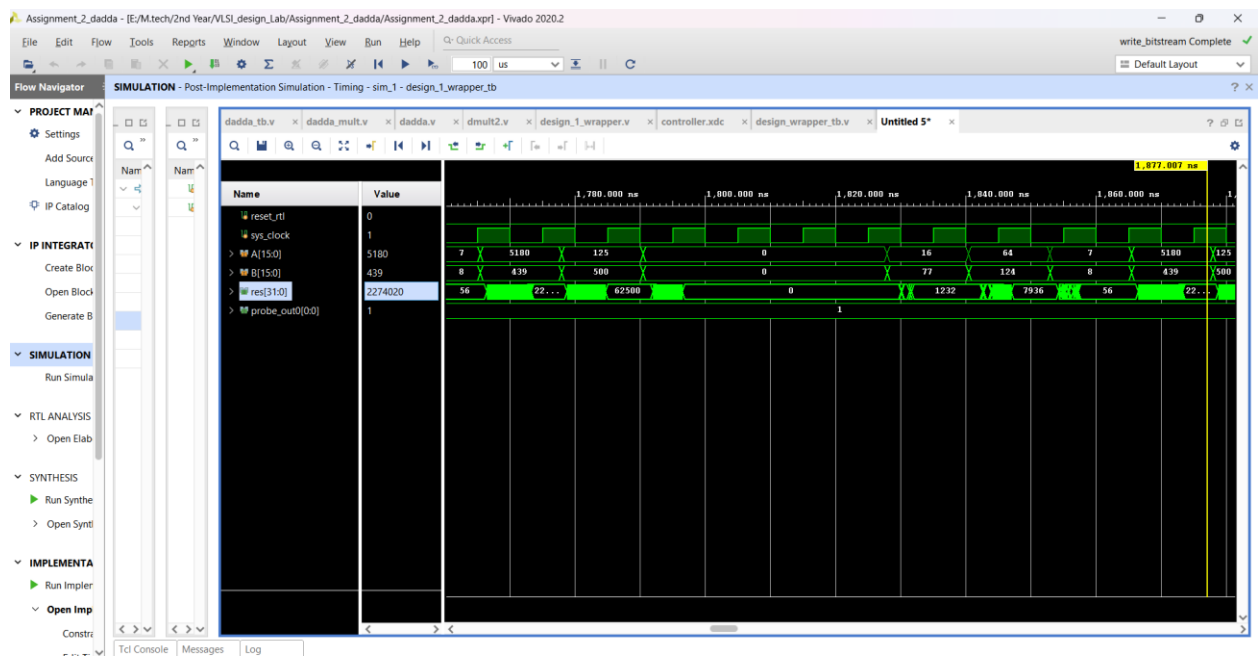

2. Dadda Multiplier Utilization

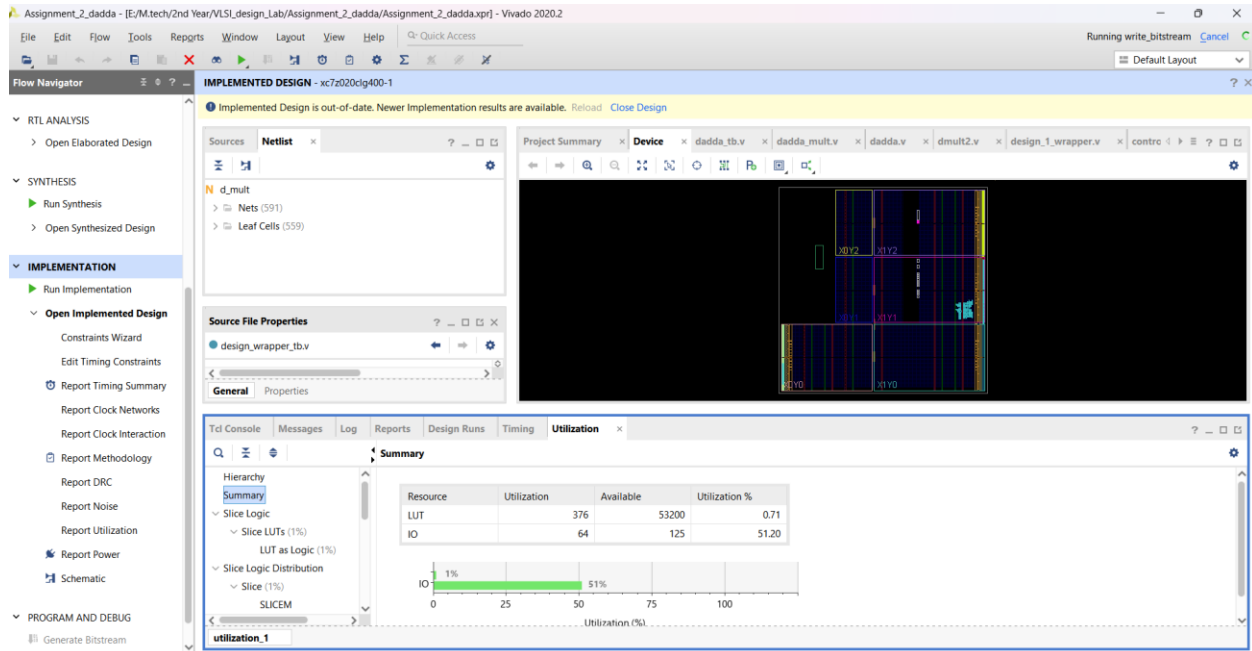

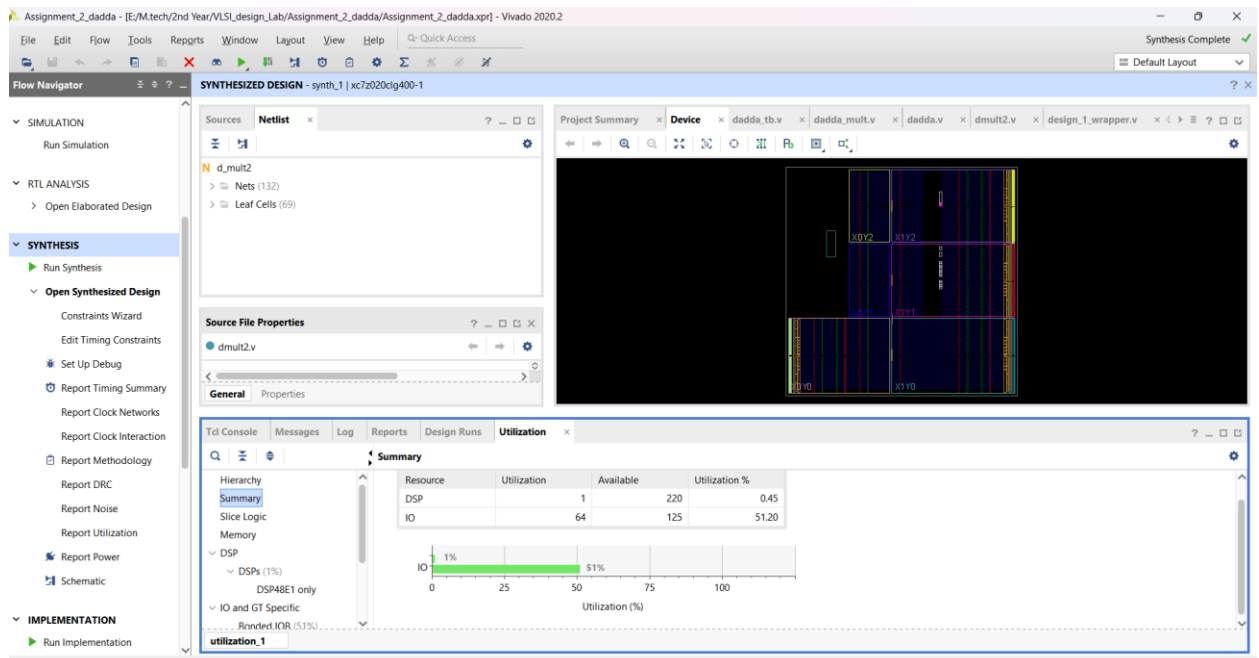3. Dadda Multiplier utilization with operator



Codes

Verilog code:

```
module d_mult(  
    input [15:0] A,  
    input [15:0] B,  
    output [31:0] res  
);  
  
    reg [30:0] pp[15:0];  
    integer i, j;  
    reg [1:0] ha_tmp;  
    reg [1:0] fa_tmp, fa_tmp1, fa_tmp2, fa_tmp3;  
    reg c_tmp, c_tmp1, c_tmp2, c_tmp3;  
    reg [31:0] s_temp, s_temp1;  
  
    task half_adder;  
        input p, q;  
        output [1:0] result;  
        begin  
            result[0] = p ^ q;  
            result[1] = p & q;  
        end  
    endtask
```

```

task full_adder;

input m, n, cin;

output [1:0] result;

begin

    result[0] = m ^ n ^ cin;

    result[1] = (m & n) | (n & cin) | (m & cin);

end

endtask

```

```

always @(*)

begin

    // Initialize partial products to zero

    for (i = 0; i < 16; i = i + 1)

        begin

            pp[i] = 31'd0;

        end

    // Partial products calculation

    for (i = 0; i < 16; i = i + 1)

        begin

            for (j = 0; j < 16; j = j + 1)

                begin

                    pp[i][j + i] = B[i] & A[j];

                end

            end

        end

```

end

// Creating triangle structure for better visualization and reducing complexity

for (j = 16; j < 31; j = j + 1)

begin

for (i = (j - 15); i < 16; i = i + 1)

begin

pp[i - (j - 15)][j] = pp[i][j];

pp[i][j] = 0;

end

end

// Reduction to d = 13

half_adder(pp[12][13], pp[13][13], ha_tmp);

pp[12][13] = ha_tmp[0];

c_tmp = ha_tmp[1];

full_adder(pp[12][14], pp[13][14], pp[14][14], fa_tmp);

half_adder(fa_tmp[0], c_tmp, ha_tmp);

pp[12][14] = ha_tmp[0];

c_tmp = fa_tmp[1];

c_tmp1 = ha_tmp[1];

full_adder(pp[13][15], pp[14][15], pp[15][15], fa_tmp1);

full_adder(pp[12][15], c_tmp1, c_tmp, fa_tmp2);

half_adder(fa_tmp1[0], fa_tmp2[0], ha_tmp);

```
pp[12][15] = ha_tmp[0];
```

```
c_tmp = fa_tmp1[1];
```

```
c_tmp1 = fa_tmp2[1];
```

```
c_tmp2 = ha_tmp[1];
```

```
full_adder(pp[12][16], pp[13][16], pp[14][16], fa_tmp1);
```

```
full_adder(c_tmp2, c_tmp1, c_tmp, fa_tmp2);
```

```
half_adder(fa_tmp1[0], fa_tmp2[0], ha_tmp);
```

```
pp[12][16] = ha_tmp[0];
```

```
c_tmp = fa_tmp1[1];
```

```
c_tmp1 = fa_tmp2[1];
```

```
c_tmp2 = ha_tmp[1];
```

```
full_adder(c_tmp2, pp[12][17], pp[13][17], fa_tmp1);
```

```
full_adder(fa_tmp1[0], c_tmp1, c_tmp, fa_tmp2);
```

```
pp[12][17] = fa_tmp2[0];
```

```
c_tmp = fa_tmp1[1];
```

```
c_tmp1 = fa_tmp2[1];
```

```
full_adder(pp[12][18], c_tmp, c_tmp1, fa_tmp1);
```

```
pp[12][18] = fa_tmp1[0];
```

```
pp[12][19] = fa_tmp1[1];
```

```
// Reduction to d = 9
```

```
half_adder(pp[8][9], pp[9][9], ha_tmp);
```

```
pp[8][9] = ha_tmp[0];
```

```
c_tmp = ha_tmp[1];
```

```
full_adder(pp[8][10], pp[9][10], pp[10][10], fa_tmp);
```

```
half_adder(fa_tmp[0], c_tmp, ha_tmp);
```

```
pp[8][10] = ha_tmp[0];
```

```
c_tmp = fa_tmp[1];
```

```
c_tmp1 = ha_tmp[1];
```

```
full_adder(pp[9][11], pp[10][11], pp[11][11], fa_tmp1);
```

```
full_adder(pp[8][11], c_tmp1, c_tmp, fa_tmp2);
```

```
half_adder(fa_tmp1[0], fa_tmp2[0], ha_tmp);
```

```
pp[8][11] = ha_tmp[0];
```

```
c_tmp = fa_tmp1[1];
```

```
c_tmp1 = fa_tmp2[1];
```

```
c_tmp2 = ha_tmp[1];
```

```
full_adder(pp[10][12], pp[11][12], pp[12][12], fa_tmp);
```

```
full_adder(pp[8][12], pp[9][12], c_tmp, fa_tmp1);
```

```
full_adder(fa_tmp[0], c_tmp1, c_tmp2, fa_tmp2);
```

```
half_adder(fa_tmp1[0], fa_tmp2[0], ha_tmp);
```

```
pp[8][12] = ha_tmp[0];
```

```
c_tmp = fa_tmp[1];
```

```
c_tmp1 = fa_tmp1[1];
```

```
c_tmp2 = fa_tmp2[1];
```

```
c_tmp3 = ha_tmp[1];
```

```
for (j = 13; j < 20; j = j + 1)
```

```
begin
```

```
    full_adder(pp[10][j], pp[11][j], pp[12][j], fa_tmp);
```

```
    full_adder(pp[8][j], pp[9][j], c_tmp, fa_tmp1);
```

```
    full_adder(fa_tmp[0], fa_tmp1[0], c_tmp1, fa_tmp2);
```

```
    full_adder(fa_tmp2[0], c_tmp2, c_tmp3, fa_tmp3);
```

```
    pp[8][j] = fa_tmp3[0];
```

```
    c_tmp = fa_tmp[1];
```

```
    c_tmp1 = fa_tmp1[1];
```

```
    c_tmp2 = fa_tmp2[1];
```

```
    c_tmp3 = fa_tmp3[1];
```

```
end
```

```
full_adder(pp[8][20], pp[9][20], pp[10][20], fa_tmp);
```

```
full_adder(fa_tmp[0], c_tmp, c_tmp1, fa_tmp1);
```

```
full_adder(fa_tmp1[0], c_tmp2, c_tmp3, fa_tmp2);
```

```
pp[8][20] = fa_tmp2[0];
```

```
c_tmp = fa_tmp[1];
```

```
c_tmp1 = fa_tmp1[1];
```

```
c_tmp2 = fa_tmp2[1];
```

```
full_adder(c_tmp, pp[8][21], pp[9][21], fa_tmp);
```

```
full_adder(fa_tmp[0], c_tmp1, c_tmp2, fa_tmp1);
```

```
pp[8][21] = fa_tmp1[0];
```

```
c_tmp = fa_tmp[1];
```

```
c_tmp1 = fa_tmp1[1];
```



```
full_adder(c_tmp, c_tmp1, pp[8][22], fa_tmp);  
pp[8][22] = fa_tmp[0];  
pp[8][23] = fa_tmp[1];
```

```
// Reduction to d = 6
```

```
half_adder(pp[5][6], pp[6][6], ha_tmp);  
pp[5][6] = ha_tmp[0];  
c_tmp = ha_tmp[1];
```

```
full_adder(pp[5][7], pp[6][7], pp[7][7], fa_tmp);  
half_adder(fa_tmp[0], c_tmp, ha_tmp);  
pp[5][7] = ha_tmp[0];  
c_tmp = fa_tmp[1];  
c_tmp1 = ha_tmp[1];
```

```
full_adder(pp[6][8], pp[7][8], pp[8][8], fa_tmp1);  
full_adder(pp[5][8], c_tmp1, c_tmp, fa_tmp2);  
half_adder(fa_tmp1[0], fa_tmp2[0], ha_tmp);  
pp[5][8] = ha_tmp[0];  
c_tmp = fa_tmp1[1];  
c_tmp1 = fa_tmp2[1];  
c_tmp2 = ha_tmp[1];
```

```
for (j = 9; j < 24; j = j + 1)
```

```
begin
```

```
full_adder(pp[8][j], pp[7][j], pp[6][j], fa_tmp);  
full_adder(pp[5][j], c_tmp, c_tmp1, fa_tmp1);  
full_adder(fa_tmp[0], fa_tmp1[0], c_tmp2, fa_tmp2);  
pp[5][j] = fa_tmp2[0];  
c_tmp = fa_tmp[1];  
c_tmp1 = fa_tmp1[1];  
c_tmp2 = fa_tmp2[1];  
end
```

```
full_adder(pp[6][24], pp[5][24], c_tmp, fa_tmp);  
full_adder(fa_tmp[0], c_tmp1, c_tmp2, fa_tmp1);  
pp[5][24] = fa_tmp1[0];  
c_tmp = fa_tmp[1];  
c_tmp1 = fa_tmp1[1];
```

```
full_adder(pp[5][25], c_tmp, c_tmp1, fa_tmp);  
pp[5][25] = fa_tmp[0];  
pp[5][26] = fa_tmp[1];
```

```
// Reduction to d = 4
```

```
half_adder(pp[3][4], pp[4][4], ha_tmp);  
pp[3][4] = ha_tmp[0];  
c_tmp = ha_tmp[1];
```

```
full_adder(pp[3][5], pp[4][5], pp[5][5], fa_tmp);  
half_adder(fa_tmp[0], c_tmp, ha_tmp);
```

```

pp[3][5] = ha_tmp[0];
c_tmp = fa_tmp[1];
c_tmp1 = ha_tmp[1];

for (j = 6; j < 27; j = j + 1)
begin
    full_adder(pp[3][j], pp[4][j], pp[5][j], fa_tmp);
    full_adder(c_tmp, c_tmp1, fa_tmp[0], fa_tmp1);
    pp[3][j] = fa_tmp1[0];
    c_tmp = fa_tmp[1];
    c_tmp1 = fa_tmp1[1];
end

```

```

full_adder(pp[3][27], c_tmp, c_tmp1, fa_tmp);
pp[3][27] = fa_tmp[0];
pp[3][28] = fa_tmp[1];

```

// Reduction to d = 3

```

half_adder(pp[2][3], pp[3][3], ha_tmp);
pp[2][3] = ha_tmp[0];
c_tmp = ha_tmp[1];

```

```

for (j = 4; j < 29; j = j + 1)
begin
    full_adder(pp[3][j], pp[2][j], c_tmp, fa_tmp);
    pp[2][j] = fa_tmp[0];

```

```

    c_tmp = fa_tmp[1];
end

pp[2][29] = c_tmp;

// Reduction to d = 2
half_adder(pp[1][2], pp[2][2], ha_tmp);
pp[1][2] = ha_tmp[0];
c_tmp = ha_tmp[1];

for (j = 3; j < 30; j = j + 1)
begin
    full_adder(pp[1][j], pp[2][j], c_tmp, fa_tmp);
    pp[1][j] = fa_tmp[0];
    c_tmp = fa_tmp[1];
end

pp[1][30] = c_tmp;

for (j = 0; j < 31; j = j + 1)
begin
    s_temp[j] = pp[0][j];
end

for (j = 0; j < 31; j = j + 1)
begin
    s_temp1[j] = pp[1][j];
end

```

```
s_temp[31] = 0;
s_temp1[31] = 0;
end
```

```
wire cout;
bkadder_32 add (
    .A(s_temp),
    .B(s_temp1),
    .cin(1'b0),
    .Y(res),
    .cout(cout)
);
```

```
endmodule
```

Testbench

```
`timescale 1ns / 1ps
```

```
module daddda_multiplier_tb;
    reg [15:0] A,B;
    wire [31:0] Y;

    d_mult dut(.A(A),.B(B),.res(Y));
```

```
    initial begin
```

```
$monitor("%d %d %d",A,B,Y);
```

```
A = 0;
```

```
B = 0;
```

```
#200 $finish;
```

```
end
```

```
always begin
```

```
A = $random;
```

```
B = $random;
```

```
#10;
```

```
end
```

```
Endmodule
```

```
Control unit:
```

```
`timescale 1ns / 1ps
```

```
module ControlUnit(
```

```
    input clka,
```

```
    input [31:0] douta,
```

```
    input start_stop,
```

```
    output reg ena,
```

```
    output reg [2:0] addra,
```

```
    output reg [15:0] a,
```

```
    output reg [15:0] b
```

```
);
```

```

always @(posedge clka) begin
    if(!start_stop)
        begin
            a <= 16'b0;
            b <= 16'b0;
            ena <= 0;
            addra <= 3'b000;
        end
    else
        begin
            a <= douta[31:16];
            b <= douta[15:0];
            ena <= 1;
            addra <= addra + 1;
        end
    end
end
endmodule

```

2. Barrel Shifter

Verilog codes :

1. Logarithmic Barrel shifter code

```
`timescale 1ns / 1ps

module Barrel_Shifter(

    input [7:0] in1, // 8-bit input data
    input [2:0] shift, // 3-bit shift amount (0 to 7)
    input LR, // Direction: 0 for left, 1 for right
    output [7:0] data_out );

    wire p1,p2,p3,p4,p5,p6,p7,p8;
    wire q1,q2,q3,q4,q5,q6,q7,q8;
    wire r1,r2,r3,r4,r5,r6,r7,r8;
    wire [7:0] out;

    // selecting Inputs based on LR

    mux2x1 m1(in1[0],in1[7],LR,p1);
    mux2x1 m2(in1[1],in1[6],LR,p2);
    mux2x1 m3(in1[2],in1[5],LR,p3);
    mux2x1 m4(in1[3],in1[4],LR,p4);
    mux2x1 m5(in1[4],in1[3],LR,p5);
    mux2x1 m6(in1[5],in1[2],LR,p6);
    mux2x1 m7(in1[6],in1[1],LR,p7);
    mux2x1 m8(in1[7],in1[0],LR,p8);
```


//

```
mux2x1 n1(p1,p2,shift[0],q1);  
mux2x1 n2(p2,p3,shift[0],q2);  
mux2x1 n3(p3,p4,shift[0],q3);  
mux2x1 n4(p4,p5,shift[0],q4);  
mux2x1 n5(p5,p6,shift[0],q5);  
mux2x1 n6(p6,p7,shift[0],q6);  
mux2x1 n7(p7,p8,shift[0],q7);  
mux2x1 n8(p8,1'b0,shift[0],q8);
```

```
mux2x1 o1(q1,q3,shift[1],r1);  
mux2x1 o2(q2,q4,shift[1],r2);  
mux2x1 o3(q3,q5,shift[1],r3);  
mux2x1 o4(q4,q6,shift[1],r4);  
mux2x1 o5(q5,q7,shift[1],r5);  
mux2x1 o6(q6,q8,shift[1],r6);  
mux2x1 o7(q7,1'b0,shift[1],r7);  
mux2x1 o8(q8,1'b0,shift[1],r8);
```

```
mux2x1 k1(r1,r5,shift[2],out[7]);  
mux2x1 k2(r2,r6,shift[2],out[6]);  
mux2x1 k3(r3,r7,shift[2],out[5]);  
mux2x1 k4(r4,r8,shift[2],out[4]);  
mux2x1 k5(r5,1'b0,shift[2],out[3]);  
mux2x1 k6(r6,1'b0,shift[2],out[2]);
```

```
    mux2x1 k7(r7,1'b0,shift[2],out[1]);  
    mux2x1 k8(r8,1'b0,shift[2],out[0]);
```

```
genvar i;  
generate  
    for (i = 0; i < 8; i = i + 1) begin : gen_block  
        assign data_out[i] = LR ? out[i] : out[7-i];  
    end  
endgenerate
```

```
endmodule
```

```
// 2-to-1 Multiplexer module  
module mux2x1 (  
    input in0, // Input 0  
    input in1, // Input 1  
    input sel, // Select signal  
    output out // Output  
);  
    assign out = sel ? in1 : in0;  
endmodule
```

Controller code:

```
module Control_Unit (  
    input clk,  
    input start_stop,  
    input left_right,  
    input wire [10:0] douta,  
    output reg [7:0] in1,  
    output reg [2:0] shift,  
  
    output reg ena,  
    output reg LR,  
    output reg [2:0] addra  
);
```

```
always @(posedge clk) begin  
    if (!start_stop) begin  
        ena <= 0;          // Disable BRAM read  
        addra <= 3'b000;    // Reset BRAM address to 0  
        in1 <= 8'b00000000; // Reset input data  
        shift <= 3'b000;    // Reset shift amount  
    end  
    else begin  
        ena <= 1;  
        in1 <= douta[10:3];
```

```
    shift <= douta[2:0];  
    LR <= left_right ? 1 : 0;  
  
    if (addra == 3'b111) begin  
        addra <= 3'b000;  
    end else begin  
        addra <= addra + 1;  
    end  
end  
end  
end  
endmodule
```

Barrel shifter Testbench

```
`timescale 1ns / 1ps
```

```
module Barrel_Shifter_tb;
```

```
    reg [7:0] in;  
    reg [2:0] shift;  
    reg LR;
```

```
    wire [7:0] data_out;
```

```
Barrel_Shifter_op uut (  
    .in1(in),  
    .shift(shift),  
    .LR(LR),  
    .data_out(data_out)  
);
```

```
initial begin
```

```
    in = 8'b00110011;  
    $display("Time\tLR\tShift\tInput\t\tOutput");
```

```
    for( LR = 0; LR<=1;LR=LR+1)
```

```
    begin
```

```
        shift = 3'b000; #5;
```

```
        $display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
        shift = 3'b001; #5;
```

```
        $display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
        shift = 3'b010; #5;
```

```
        $display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
        shift = 3'b011; #5;
```

```
$display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
shift = 3'b100; #5;
```

```
$display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
shift = 3'b101; #5;
```

```
$display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
shift = 3'b110; #5;
```

```
$display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```

```
shift = 3'b111; #5;
```

```
$display("%d\t%b\t%b\t%b\t%b", $time, LR, shift, in, data_out);
```


```
end
```

```
$finish;
```


```
end
```

```
endmodule
```


1. Behavioral simulation

 


2. Post-Implemented Timing Simulation

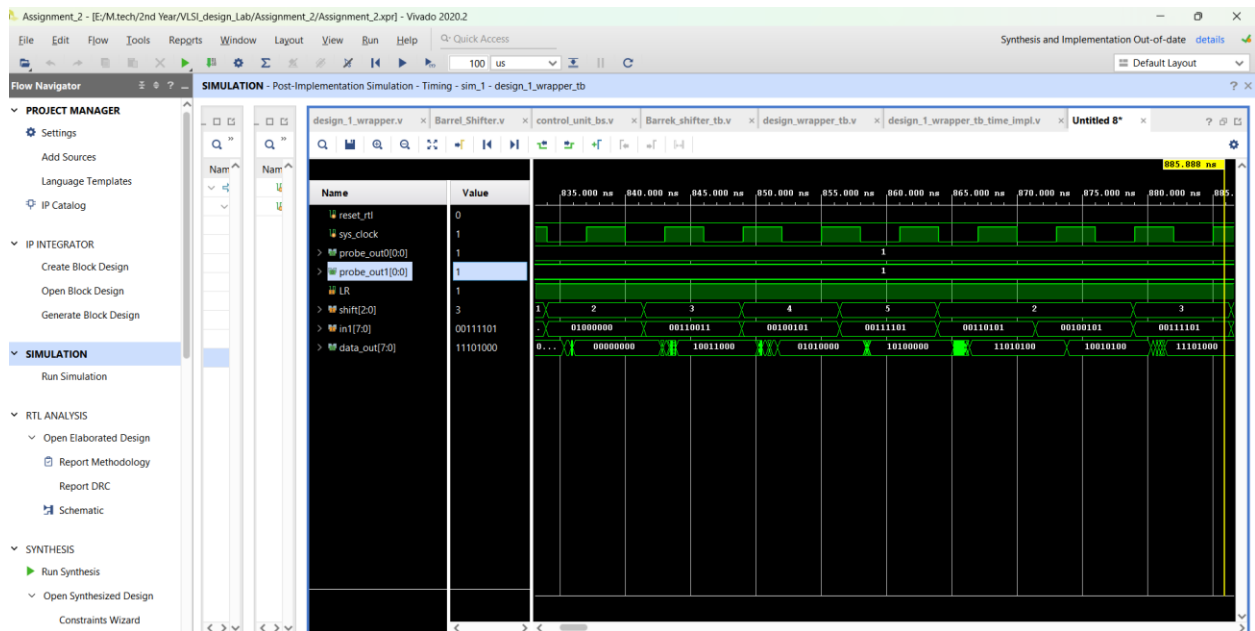


3. Barrel Shifter with Operator

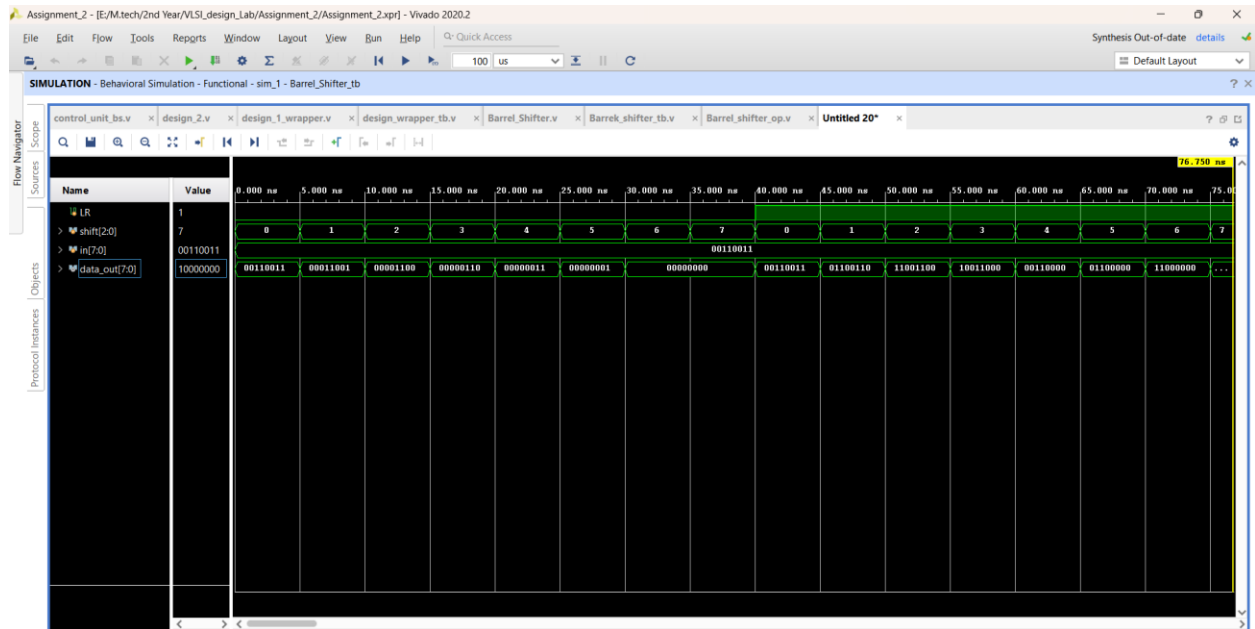


4. Block diagram

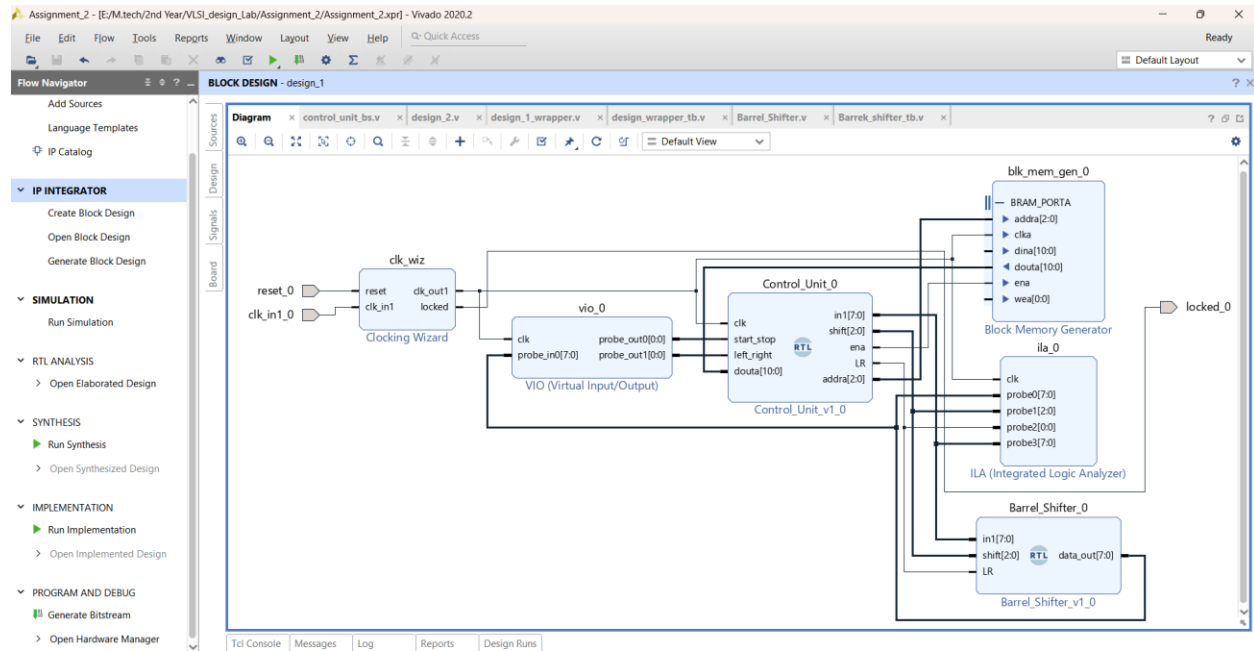

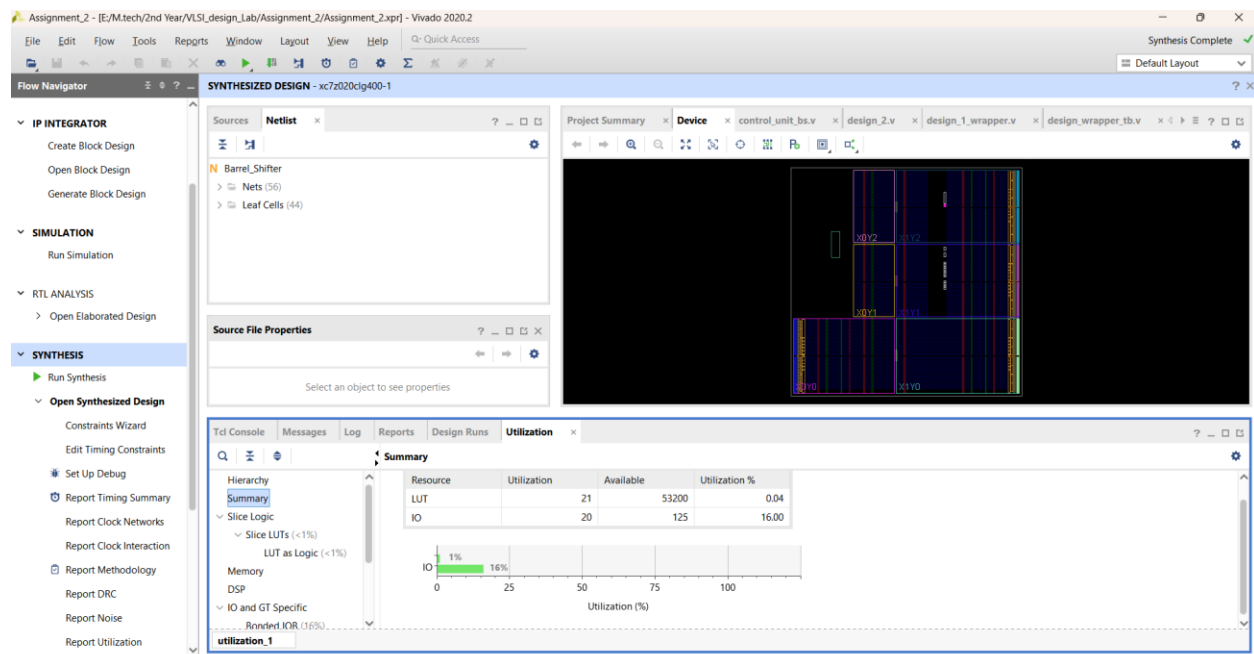5. Logarithmic Barrel shifter utilization



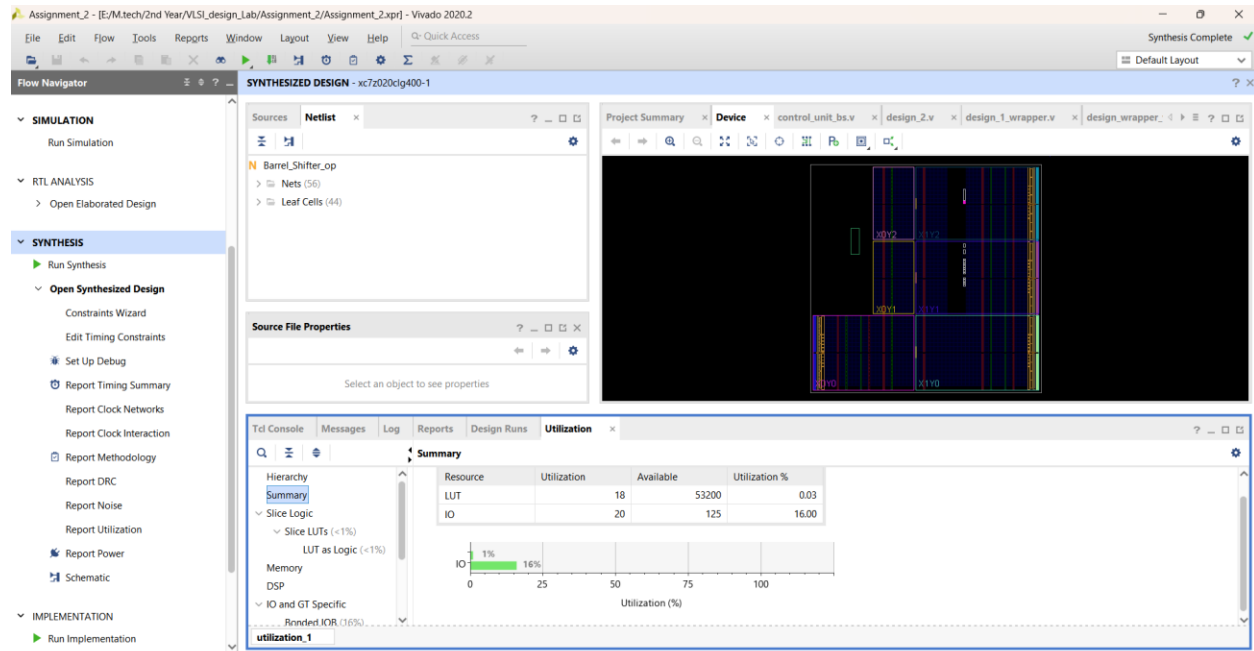6. Barrel shifter utilization with operator.



Inference : **Utilization of barrel shifter without operator is little more(3 more LUTs) then when implemented using shift operator.**